

- (b) Find Thevenin's equivalent circuit at terminals a-b for circuit shown in Figure 9. (10)

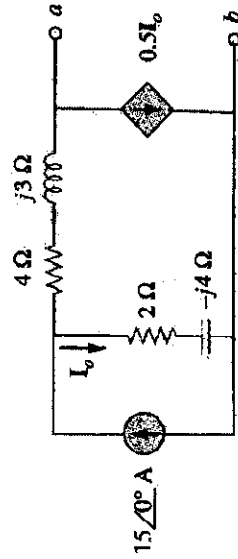


Figure 9

Your Roll No.....

Sr. No. of Question Paper : 1045

C

Unique Paper Code : 2512041102

Name of the Paper : Basic Circuit Theory

Name of the Course : B.Sc. (H) Instrumentation

Semester : I

Duration : 3 Hours

Maximum Marks : 90

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. There are **seven** questions in all, out of which you have to attempt **five** questions. Question **1** is compulsory.
3. **All** questions carry equal marks.
4. Use of Non-Programmable Scientific Calculator is allowed.

1. (a) What is the lower cut off frequency of High Pass RC filter if $R = 5K$ and $C = 0.01\mu F$? (3)

(1000)

P.T.O.

- (b) Write the expression of current through the inductor for source free RL circuit. Also plot the current transient assuming I_0 be the initial current through inductor. (3)
- (c) Define Instantaneous, Peak to Peak, Root Mean Square and Average Values of current. (3)
- (d) Explain the Reciprocity Theorem with example. (3)
- (e) Explain Voltage-Current relationship in Resistor, Inductor and Capacitor. (3)
- (f) Explain resonance in Series RLC Circuits, Frequency Response of Series RLC Circuits and Quality (Q) Factor. (3)
2. (a) Evaluate the value of R so that the maximum power is delivered to R for the circuit shown in Figure 1. Determine the maximum power delivered to R and the power efficiency of circuit under maximum power condition. (9)

- (b) Evaluate the Z-parameters for the circuit shown in Figure 8. (9)

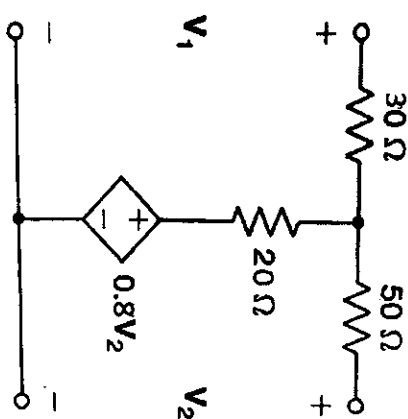


Figure 8

7. (a) In a series RLC circuit, if $R=4\Omega$, $L=25\text{mH}$, $C=0.625\mu\text{F}$ and peak source voltage $V_s=100\text{V}$ then evaluate: (8)
- (i) Resonant frequency (f_r)
- (ii) Quality factor (Q)
- (iii) Bandwidth (B)
- (iv) Impedance at Resonance

5. (a) Determine the range of frequencies that will be passed by a series RLC band pass filter with $R=10\ \Omega$, $L=12.5\ \text{mH}$ and $C=0.8\ \mu\text{F}$. Find the quality factor. Explain how the same combination can be used to design a series RLC band stop filter. Also, draw the frequency response for both cases. (9)

- (b) Define Instantaneous power, average power, reactive power, complex power and power factor. (9)

6. (a) Find time-period, frequency, avg value, rms value, form factor and peak factor of the waveform shown below in Figure 7. Also, find the instantaneous, average and total power. (9)

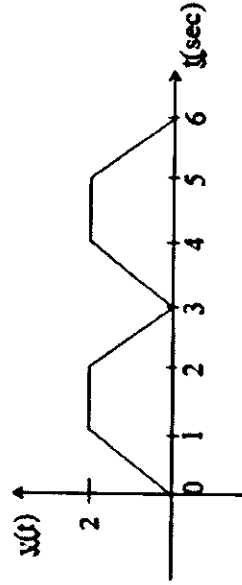


Figure 7

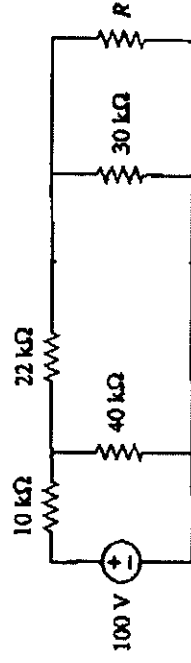


Figure 1

- (b) Find the voltages at node 1 & 2 for the circuit shown in Figure 2. (9)

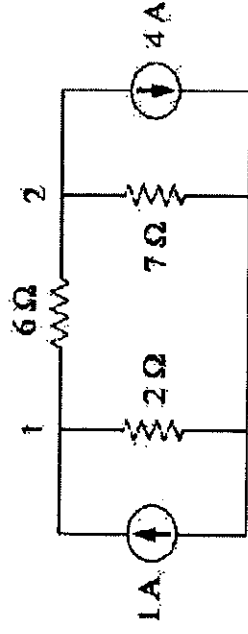


Figure 2

3. (a) Obtain the z-parameters and transmission-parameters for the circuit shown in Figure 3. (9)

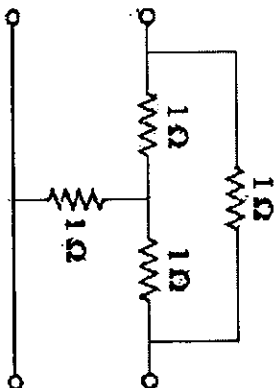


Figure 3

- (b) Find the mathematical expression for the current $i_L(t)$ for the circuit shown in Figure 4 where the switch was closed at $t=0$ s. Assume that current through inductor is zero initially. (9)

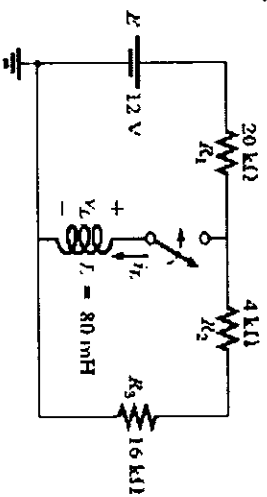


Figure 4

4. (a) Find the voltage developed across resistor 8Ω using superposition theorem for the circuit shown in Figure 5. (10)

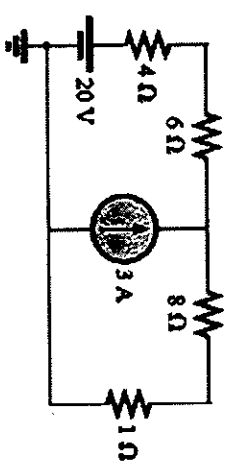


Figure 5

- (b) Find the equivalent resistance seen by the voltage source using star-delta conversion for the circuit given in Figure 6 and also find the total current flowing in the circuit. (8)

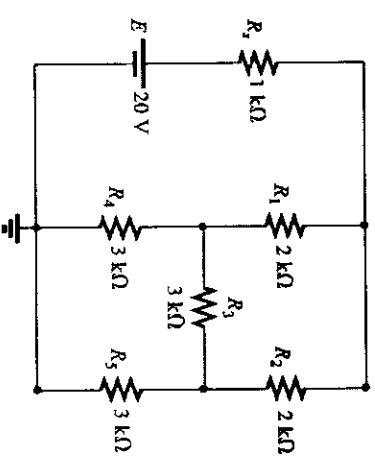


Figure 6