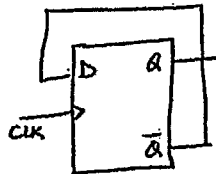


- (b) Design a MOD10 asynchronous counter. Explain its working using JK Flip-Flops. (6)
- (c) With the logic diagram explain the working of a 4-bit serial-in, parallel-out shift register. (6)
6. (a) State and prove commutative and Associative laws of Boolean algebra. (6)
- (b) With the help of a logic diagram explain a 4-bit binary parallel Adder. (6)
- (c) Distinguish between :
- Combinational and sequential logic
 - Multiplexer and Demultiplexer
- (6)
7. (a) Write the VHDL code for 3 to 8 decoder. (6)
- (b) Assume the clock frequency in the circuit to be 1KHz. Write the truth table. Draw the output waveforms at Q and $\bar{Q}$. What is the frequency of the output waveform?



- (c) Draw the logic diagram for a 4-bit Johnson counter. Also draw the timing diagram and the sequence. (6)

(1000)

[This question paper contains 4 printed pages.]

Your Roll No.....

Sr. No. of Question Paper : 6040

H

Unique Paper Code : 2514001201

Name of the Paper : Digital System Design

Name of the Course : B.Sc. (H) Electronics –
Generic Elective (GE)

Semester : II

Duration : 3 Hours

Maximum Marks : 90

Instructions for Candidates

- Write your Roll No. on the top immediately on receipt of this question paper.
- Attempt **five** questions in all.
- Question No. 1 is compulsory.
- Use of non-programmable scientific calculator is allowed.

- (a) Obtain the truth table of the function $f = (A+B)(\bar{B}+C)$ and implement it with logic gates. (3)

(b) Convert decimal 258 into its binary, hexadecimal and octal code. (3)

P.T.O.

- (c) State and prove De Morgan's theorem by taking an example. (3)
- (d) An 8bit shift register contents are 11000011. What are the contents after 3 right shifts? Assume $D_{in} = 1$. (3)
- (e) If the clock frequency to a 3-bit ripple counter is 12 kHz, what will be the frequency of the LSB (Q0), Q1 and Q2(MSB). (3)
- (f) What is the difference between a synchronous and asynchronous counter? (3)

2. (a) Do the following :

- (i) Subtract 14_{10} from 46_{10} using the 8-bit 2's complement arithmetic.
- (ii) Add -75_{10} to $+26_{10}$ using the 8-bit 2's complement arithmetic. (6)

(b) Simplify the following expression using Boolean algebra and implement them with NAND gate :

$$F = \overline{A}BC + B + B\overline{D} + AB\overline{D} + \overline{A}C \quad (6)$$

(c) Express the following function in a sum of product and a product of Sum.

$$F = AB + AC + \overline{B}C \quad (6)$$

3. (a) Convert the following :

(i) 100110110_2 to Gray Code

(ii) 110110010_2 to BCD (6)

(b) Reduce the expression using K-map method and implement with universal gate NAND logic :

$$F = \sum m(0,2,3,4,6,8,10,11,12,14) \quad (6)$$

(c) Show that

$$(i) (A \text{ xor } B) = A\overline{B} + \overline{A}B$$

$$(ii) (A + \overline{B})(\overline{A} + B) = A \text{ xnor } B$$

and construct the corresponding logic diagram.

(6)

4. (a) Design a 4-bit Gray to Binary code converter.

(6)

(b) Explain with the help of logic diagram and functional table a 4-input multiplexer. (6)

(c) Implement the function $f(A,B,C) = \sum(0,2,5,7)$ with a decoder and an OR gate (6)

5. (a) Draw and explain the working of JK Flip-Flop using NAND gates. Give its truth table. What is race around condition and how it can be avoided?

(6)