

- (b) What are the output voltages caused by logic 1 in each bit position in an 8-bit ladder if the input level for 0 is 0 V and that for 1 is +10 V? (6)
- (c) Write the sketch for the blinking LED with a delay of 5 seconds. (6)
6. (a) Write down the four applications of Arduino. (4)
- (b) Explain the difference between an Arduino and a microcontroller. (4)
- (c) How is the piezo-electric effect seen in some crystals used to make measurements? Explain with the help of a suitable diagram and equivalent circuit. (10)
7. (a) Explain the working of 555 timer as Astable multivibrator with the help of block diagram. (8)
- (b) Design an astable multivibrator using 555 timer to generate a square wave of 5 KHz with 70% duty cycle. (6)
- (c) Discuss the application of monostable multivibrator. (4)

(1000)

[This question paper contains 4 printed pages.]

Your Roll No.....

Sr. No. of Question Paper : 3030

I

Unique Paper Code : 2514002001

Name of the Paper : Electronic Circuits and Interfacing

Name of the Course : B.Sc. (Hons. / Prog.) All Courses (GE III)

Semester : III

Duration : 3 Hours

Maximum Marks : 90

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
 2. Question No. 1 is compulsory.
 3. Attempt **five** questions in all.
 4. All questions carry equal marks.
-
1. (a) Why is an open loop operational amplifier unsuitable for linear applications? (3)
 - (b) What is the significance of feedback in Operational amplifiers? What is its effect on parameters and characteristics? (3)

P.T.O.

- (c) What are the differences between active and passive transducers (3)
- (d) What is the function of ADC? Write down one application. (3)
- (e) What is an all pass filter and where is it used? (3)
- (f) A 6-bit DAC has a step size of 50 mV. Determine the full-scale output voltage and the percentage resolution. (3)
2. (a) How can we obtain a subtractor and a summing amplifier using a basic differential op-amp configuration? Explain with the help of circuit diagrams. (6)
- (b) Design a differentiator to differentiate a signal having frequency 1 KHz. Draw output waveforms of a differentiator for inputs (i) triangular wave (ii) square wave. (6)
- (c) Explain the working of Schmitt trigger and plot its hysteresis curve. (6)

3. (a) For a band pass filter with $f_L = 200$ Hz and $f_H = 1$ KHz and pass band gain = 4. Calculate the value of Q and also specify type of band pass filter. (6)
- (b) Design a Wein Bridge Oscillator to generate a signal of frequency 500 Hz. (6)
- (c) Describe the working of a voltage to current converter circuit. (6)
4. (a) What are primary and secondary transducers? How are they different from each other? (6)
- (b) A resistive potentiometer transducer is used for the measurement of displacement. The total length of the resistive track is 10 cm, the total resistance is 500Ω , and the supply voltage is 15 V. When the wiper is 7.5 cm away from the upper end, calculate the output voltage. (6)
- (c) Write a short note on the Hall Effect Sensor. (6)
5. (a) Explain the working of R-2R Ladder type Digital to Analog converter. (6)