

[This question paper contains 4 printed pages.]

Your Roll No.....

Sr. No. of Question Paper : 9230

J

Unique Paper Code : 2513012006

Name of the Paper : Network Synthesis

Name of the Course : **B.Sc. (Hons.) Electronic Science NEP**

Semester : IV

Duration : 3 Hours

Maximum Marks : 90

Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. There are **seven** questions in all, out of which you have to attempt any **five** Questions.
3. **All** questions carry equal marks
4. Question No. 1 is compulsory.
5. Use of simple calculator is allowed.

1. (a) State Initial and Final Value Theorem. (3)

(b) Define: (3)

(i) Symmetrical Two Port Network

(ii) Reciprocal Two Port Network

(c) Define a Causal System. (3)

(d) The given impedance function is not an LC- admittance. Give reason. (3)


$$Y(s) = \frac{Ks(s^2 + 4)}{(s^2 + 1)(s^2 + 3)}$$

(e) Determine the number of zeros of transmission for a network with the given transfer admittance. (3)


$$Y(s) = \frac{s^2}{(s^3 + 3s^2 + 4s + 2)}$$

P.T.O.

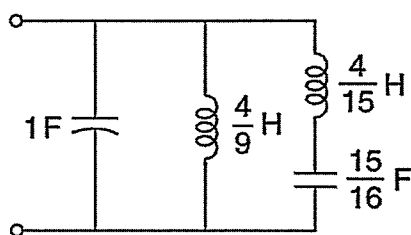- (f) Find the driving point impedance $Z(s)$ of the given network (3)



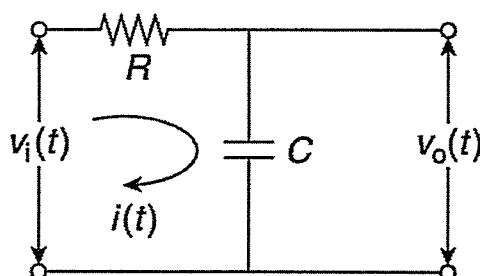2. (a) Derive the transformation expression for an inductor and a capacitor in s domain with initial current I_0 and initial charge V_0 respectively. Draw the equivalent circuits also. (6)
- (b) Determine the voltage transfer function for a RC circuit as shown. Also, find the voltage impulse response of the same. (6)



- (c) Deduce the Transmission or ABCD parameters for a two port network. (6)
3. (a) Write the conditions of the system function $H(s)$ that must be satisfied for the network to be stable. (4)
- (b) Test if the given polynomials are Hurwitz. (6)
- (i) $Q(s) = s^4 + 8s^2 + 32$
- (ii) $Q(s) = s^3 + 6s^2 + 12s + 8$
- (c) Determine whether the function $F(s)$ is a positive real function (PRF). (8)

$$F(s) = \frac{s^2 + 6s + 5}{s^2 + 9s + 14}$$

Give the significance of PRF.

4. (a) List all the properties of RL impedance functions. (4)

- (b) Synthesize the network with the given impedance function using: (14)

- (i) Foster form-I and
(ii) Cauer form-II

$$Z(s) = \frac{2(s+1)(s+3)}{(s+2)(s+6)}$$

5. (a) Synthesize the given transfer impedance function with a 1 ohm termination. (6)

$$Z_{21} = \frac{2}{(s^3 + 3s^2 + 4s + 2)}$$

Also, identify the type of filter synthesized.

- (b) Derive the equation for a lattice network to be a constant resistance network. (7)

$$Z_a Z_b = R^2$$

- (c) Draw the characteristics of an ideal low pass filter. Compare the Butterworth filters with Chebyshev filters. (5)

6. (a) Write the characteristic equation for the given network function. (8)

$$Z(s) = \frac{(2s^2 + 80s + 1000)}{s(s+10)(s+30)}$$

And hence, draw the pole-zero diagram for the same and infer about the stability of the system.

- (b) Find the limits of K so that the polynomial $s^3 + 14s^2 + 56s + k$ may be Hurwitz. (4)

- (c) Synthesize the network with the given positive real impedance using basic synthesis procedure. (6)

$$Z(s) = \frac{(6s^3 + 3s^2 + 3s + 1)}{6s^3 + 3s}$$


7. (a) Differentiate between : (4)

- (i) Foster Form-I and Foster Form-II
- (ii) Cauer Form-I and Cauer Form- II

(b) Show whether the following driving point functions represent a R-L or a R-C network. Give reasons for your answer. (4)

$$Z(s) = \frac{(s+6)(s+2)}{(s+1)(s+5)}$$

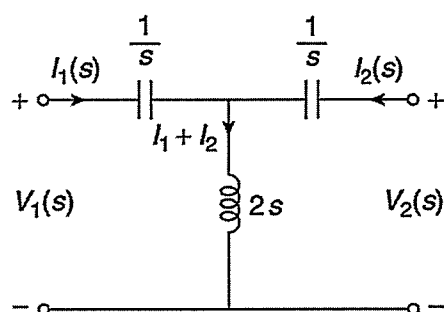(c) Find the h parameters for the given network. (5)



(d) Determine the following for a two port network terminated by a load resistor R. (5)

- (i) Z_{11}
- (ii) Z_{21}