

- (c) Define Resonance in Series RLC Circuit. Obtain the expressions for resonant frequency ω_0 , the two half power frequencies ω_1 and ω_2 , bandwidth B and the quality factor Q for the Series RLC Circuit. (6)

[This question paper contains 12 printed pages.]

Your Roll No.....

Sr. No. of Question Paper : 5824

K

Unique Paper Code : 2512011102

Name of the Paper : Circuit Theory and Network Analysis

Name of the Course : B.Sc. (H) Electronics (DSC II)

Semester : I


Duration : 3 Hours

Maximum Marks : 90



Instructions for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. There are **seven** questions in all, out of which you have to attempt any **five** questions
3. **All** questions carry equal marks.
4. **First** Question is Compulsory.
5. Use of Non-Programmable Scientific Calculator is allowed.

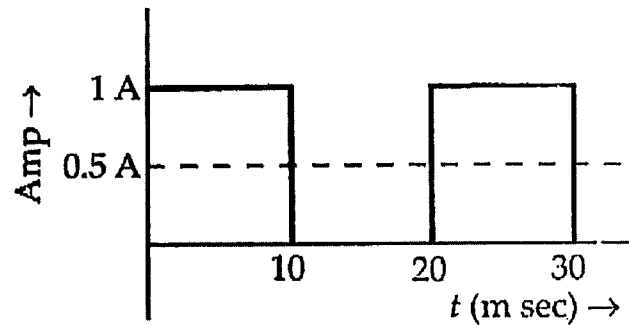
1. (a) Differentiate between an Ideal and Practical voltage source with the help of symbolic representation and I-V characteristics. (3)
- (b) Find the rms value of the current waveform shown in figure below. (3)



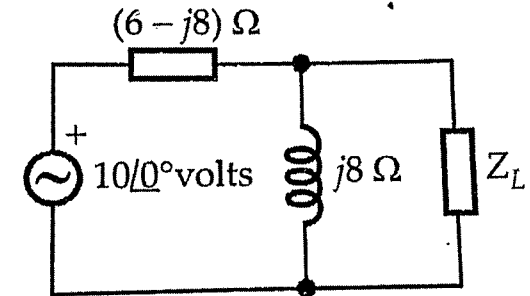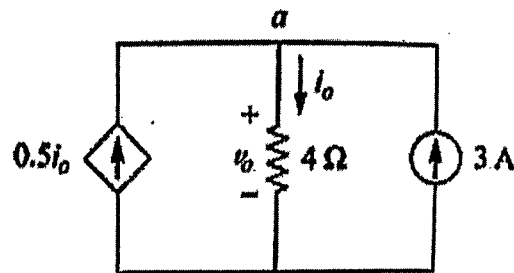
- (c) Calculate the current i_o through 4Ω resistor for the circuit given below. (3)



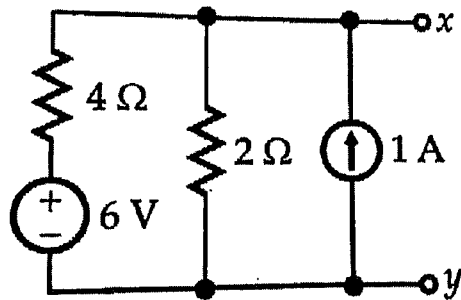7. (a) Design a Low-Pass RC Filter having cut-off frequency $f_c = 2.4$ KHz. Draw the frequency response of the designed circuit. (6)
- (b) A Series circuit comprises a 10Ω resistance, a $5\mu F$ capacitor, and a variable inductance L . The supply voltage is $20\angle 0^\circ$ volts at a frequency of 318.3 Hz. The inductance is adjusted until the p.d. across the 10Ω resistance is a maximum. Determine for this condition (6)
- the value of inductance L ,
 - the p.d. across each component, and
 - the Q-factor.



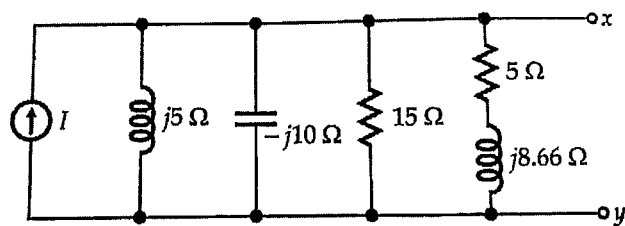
- (b) For $I = 33 \angle -13^\circ$ Amp, find the Thevenin equivalent of the following circuit. (8)



- (c) Find the value of load impedance in the following circuit to extract maximum power from the source. (4)

- (d) Explain the Principle of Duality in electrical networks. Give one example of a dual pair. (3)
- (e) Differentiate between the ideal and practical response of High Pass RC Filter. (3)
- (f) Write down the formulae for converting a delta network (consisting of Z_1 , Z_2 and Z_3) into a star network (consisting of Z_A , Z_B and Z_C). (3)

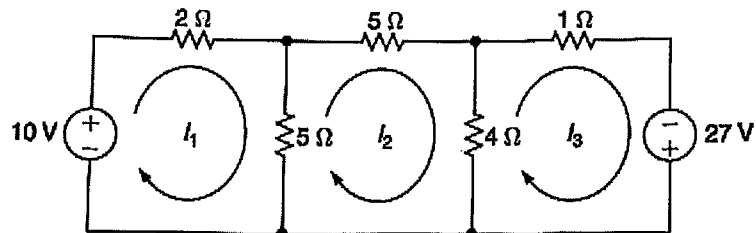
2. (a) Apply the mesh current method to the network shown below and write the matrix equations by inspection. Obtain current I_1 . Also obtain contribution of each source to I_1 . (6)




5824

4

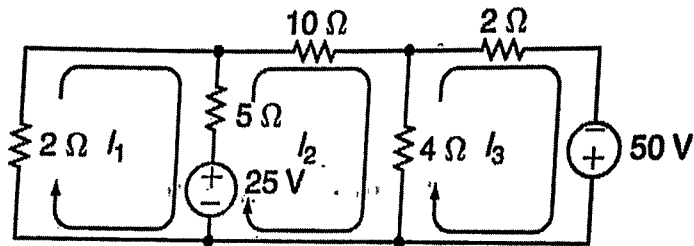- (b) Solve for the mesh currents in the network shown below by using node voltage method. (6)



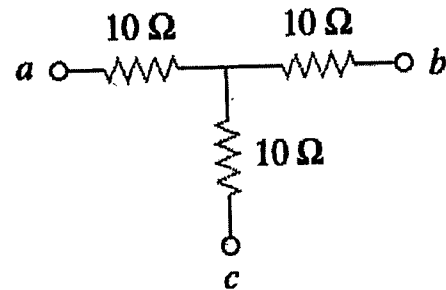- (c) (i) Convert the following Star network to its equivalent Delta network. (6)




5824

9


- (b) State and prove Maximum Power Transfer theorem. (8)

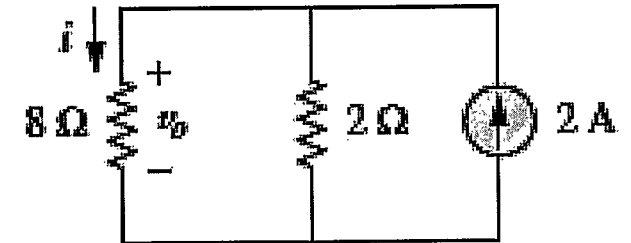- (c) Calculate the voltage v_o across 8 ohm resistor by transforming the current source to voltage source in the following circuit. (4)




6. (a) Find Millman's equivalent for the left of the terminals x-y after converting current source to voltage source. (6)


P.T.O.

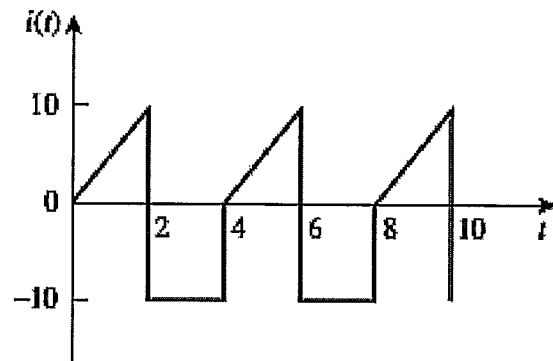

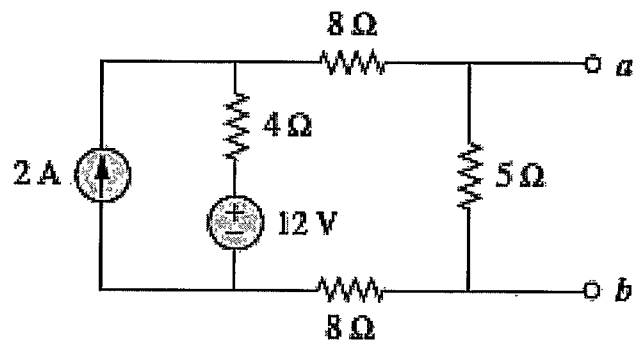5. (a) Find the Norton equivalent of the following circuit across terminals a-b. (6)



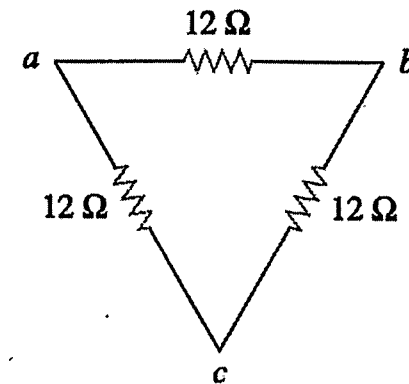
- (ii) Convert the following Delta Network to its equivalent Star network.




3. (a) What are the various types of controlled sources. Explain briefly using symbolic representation. (4)
- (b) In the circuit shown below, what is the power absorbed by each element. (7)

5824

6

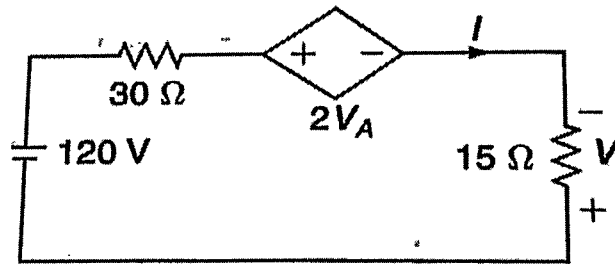

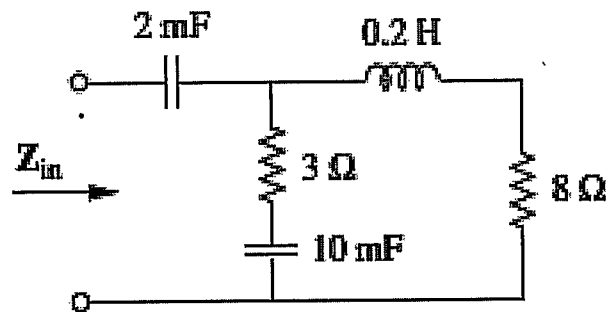
- (c) Determine the value of input impedance of the following circuit at $\omega = 50$ rad/s. (7)




4. (a) In the following circuit, find the (i) average power supplied by the source, (ii) average power absorbed by the resistor and (iii) average power absorbed by the capacitor. (6)

5824

7

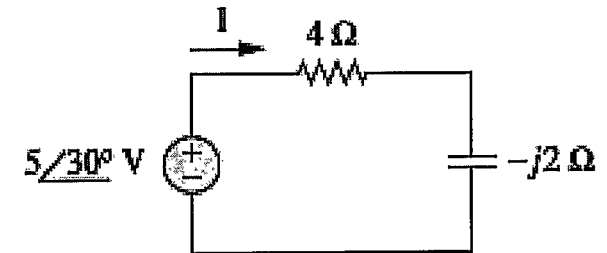

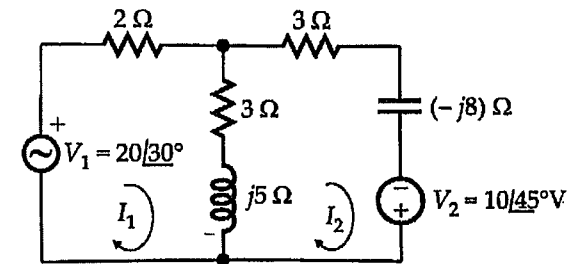- (b) Find the value of current (I_2) flowing through capacitor in the following circuit using Mesh analysis. (6)



- (c) Find the rms value of the current waveform shown in figure below (6)

P.T.O.