

[This question paper contains 2 printed pages.]

Sr. No. of Question Paper : 2052

Your Roll No.....

Unique Paper Code: 2512011202

L

Name of the Paper: Digital Electronics

Name of the Course: B.Sc(H) Electronics (Core)

Semester: II (Under NEP UGCF mode)


Duration: 03 Hour

Maximum Marks: 90

Instruction for Candidates

1. Write your Roll No. on the top immediately on receipt of this question paper.
2. Attempt any 5 questions in all, including question 1 which is compulsory.
3. Use of Scientific Calculator is allowed.

 - Q1 (a) Convert $(230.3)_{10} = ()_2 = ()_8 = ()_{16}$ (3)
- (b) Simplify the expression using Boolean Algebra. (3)
 $Y = [(XY' + XYZ)' + X(Y + XY')]$
- (c) 1101010 is a signed binary number. Determine its decimal value in (3)
(i) sign magnitude form and (ii) 2s complement form.
- (d) The waveforms as shown in the figure below are applied to the edge- (3)
triggered S-R flip-flop. Draw the output waveform.



- (e) What are PRESET and CLEAR inputs? (3)
- (f) Define the following: (3)
(i) Fan-in
(ii) Fan-out
(iii) Noise Margin
- Q2 (a) Prove that (6)
(i) $AB + (AC)' + AB'C(AB + C) = 1$
(ii) If $A + B = A + C$ and $A' + B = A' + C$, then $B = C$
(iii) Without reducing convert the following expression into NAND logic $(1 + A)(AC)$
- (b) Perform the following using binary multiplication and computer method of multiplication (6)
 $(1001)_2 \times (1101)_2$
- (c) Detect and correct errors in the following even parity Hamming code words (6)
(i) 1101010
(ii) 0111101

- Q3 (a) Minimize the expression using K-maps and implement it using NAND- (6)
NAND logic
 $Y = \prod M(0,1,3,5,6,7,10,14,15)$
- (b) Design a combinational logic circuit with 4 input variables that will (6)
produce logic 1 output when the number of 1s in the output is even.
- (c) Implement the given function using 8x1 Multiplexer. (6)
 $F = \sum m(0,1,3,4,6,8,10,11,12,15)$
- Q4 (a) Draw the circuit of a BCD adder and explain its working. (6)
- (b) Implement given expressions using a decoder (6)
 $Y1 = \sum m(0,2,6,8,10)$
 $Y2 = \sum m(4,5,6,8)$
 $Y3 = \sum m(10,11,13)$
 $Y4 = \sum m(6,7,9,11,15)$
- (c) Use tabular method to minimize the expression (6)
 $F = \sum m(0,2,3,6,7,8,9,10,13)$
- Q5 (a) Convert a SR flip-flop into a T flip-flop. Derive the required input (6)
equations using excitation and characteristic tables and draw the logic
circuit diagram.
- (b) Why are edge-triggered flip-flops preferred over level-triggered flip- (6)
flops? Explain the problem of race-condition in JK flip flop and how it
can be eliminated.
- (c) Design a type D counter that goes through states 0, 1, 2, 4, 0, The (6)
unused states must always go to zero (000) on the next clock pulse.
- Q6 (a) Draw the logic diagram of 4 bit serial in serial out shift register and (6)
explain its working with an example.
- (b) Design a synchronous MOD-10 (Decade) counter using T flip-flop. (6)
Show how the counter resets automatically.
- (c) Obtain the excitation table, state table and state diagram representing the (6)
operation of a D flip-flop. Also, write its characteristic equation based
on the state table.
- Q7 (a) Explain the working principle of a Successive Approximation ADC with (6)
diagram.
- (b) What is the difference between ROM and RAM. Mention any three (6)
different types of ROM and explain their working.
- (c) Show how the FPLA can be programmed to implement a full subtractor. (6)